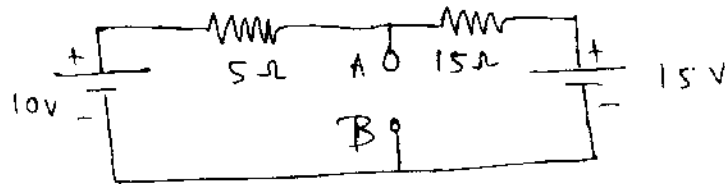


8. a) In the DC circuit, resistors $R_1 = 10\Omega$, $R_2 = 20\Omega$ and $R_3 = 100\Omega$ are connected, in turn, to terminals AB. Determine the power delivered to each resistor. 10



- b) Find I_1 , I_2 and I_T .


Draw the phasor diagram for the 3 currents.

Determine z_{eq} from V/I .

Hence compare this z_{eq} with equivalent impedance obtained by

$$z_{eq} = \frac{z_1 z_2}{z_1 + z_2} \text{ where}$$

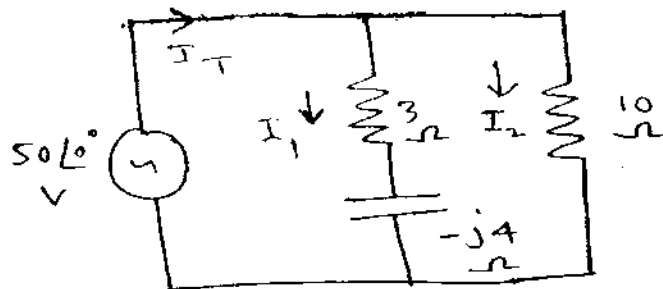z_1 and z_2 are the impedances of the 2 loops. 10



BACHELOR OF COMPUTER Sc. ENGG. EXAMINATION, 2009
(1st Year, 1st Semester)

CIRCUITS AND NETWORK THEORY

Time : Three hours

Full Marks : 100


Answer any *five* questions.

1. a) In the given circuit, the voltage function $v(t) = 100 \sin \omega t$ volts.

Find

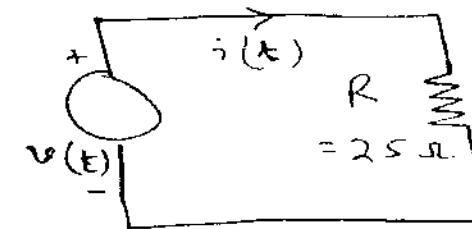- (i) current, $i(t)$, (ii) instantaneous power, $p(t)$,
(iii) average power, P .

Show graphically the variations of $v(t)$, $i(t)$ and $p(t)$.




- b) A capacitor of C farads has an applied voltage $v(t) = V_m \sin \omega t$ volts across it. Find the expressions for :
- (i) current, $i(t)$, (ii) power, $p(t)$, (iii) charge $q(t)$,
(iv) stored energy, $w(t)$.

[TURN OVER]


(2)

Also plot all the functions against time. Assume zero stored energy in the electric field at $t = 0$. 5+5

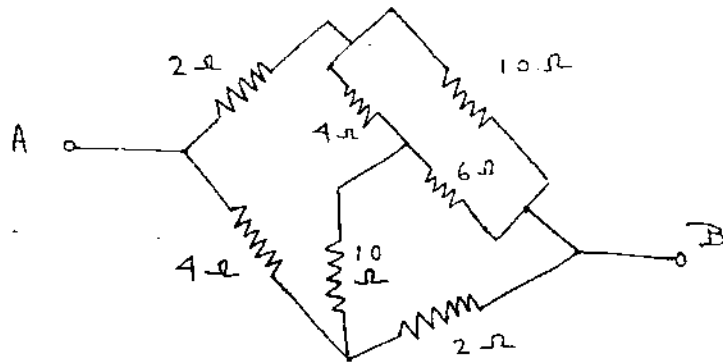2. a) Find the value of a single resistance to replace the network between terminals A and B : 10



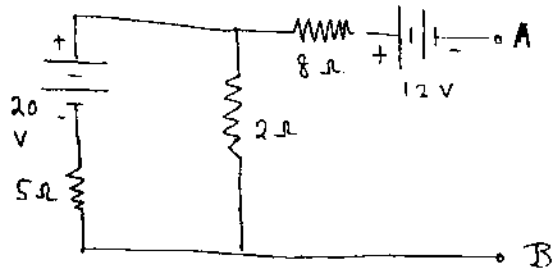
- b) Obtain (i) Thevenin Equivalent circuit and (ii) Norton Equivalent circuit at terminals AB : 5+5




(5)

- c) Find $F(s)$ for the sawtooth $f(t)$;

7

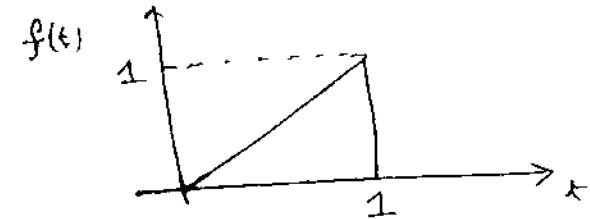

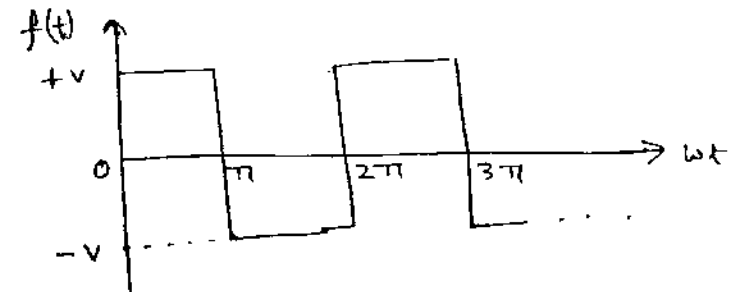7. a) What is the difference between Fourier Series and Fourier Transform ? 3
- b) Define even and odd functions from the point of view of Fourier Series. Determine which of the following functions are even and which are odd :
- (i) $f(x) = 2 + x^2 + x^4$
 - (ii) $f(x) = \sin x$
 - (iii) $f(x) = x + x^3 + x^5 + x^7$ 7
- c) Find the Fourier Series (Trigonometric) for the square wave shown and plot the line spectrum : 10




[TURN OVER]

(3)


3. a) Obtain the Thevenin equivalent circuit at terminal AB :

10

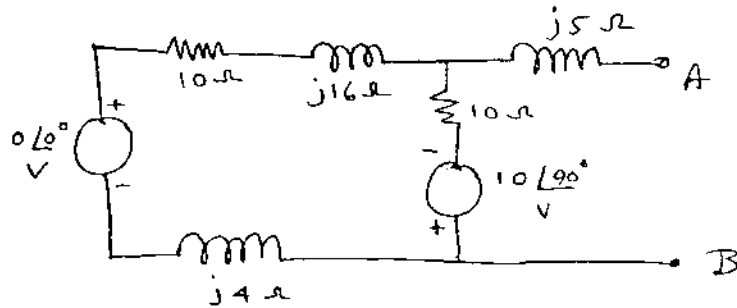


- b) For the given network, find the voltage across A and B.
(V_{AB}) :

10

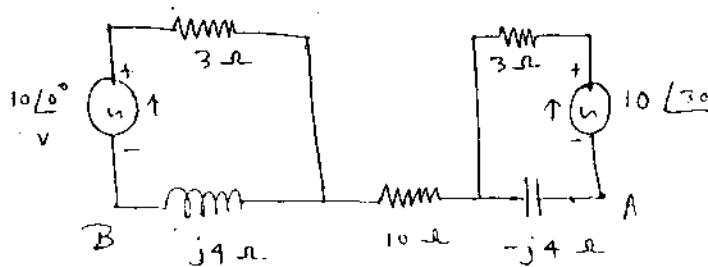

4. a) Find the current drawn from the 2 volt battery in the network :

10

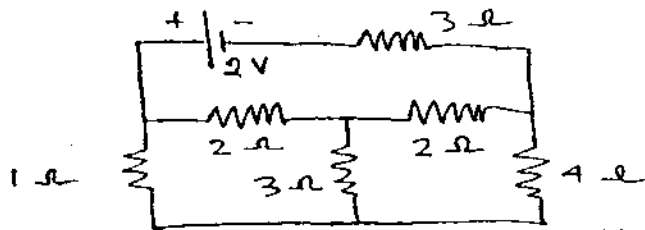

[TURN OVER]

(4)

- b) Draw the practical characteristics of (i) a LPF ; (ii) a HPF; (iii) a BPF and (iv) a notch filter. Indicate clearly the corner frequencies and the bandwidths on the diagrams. When do circuits use BPF and when are notch filters used ? Explain the Roll-off rate. 6+2+2

5. a) Prove that ωL and $1/\omega C$ have dimensions of ohms. 4

- b) A series RC circuit with $R = 10 \Omega$, has an impedance with an angle of -45° at $f_1 = 500$ Hz. Find the frequency for which the magnitude of the impedance is (a) twice that at f_1 and (b) one-half that at f_1 . 8

- c) A series circuit consists of $R = 1\Omega$, and inductive reactance $jX_L = j4$ ohms and a third impedance Z of $\vec{V} = 50\angle45^\circ$ volts and $\vec{I} = 11.2\angle108.4^\circ$ A find out Z . 8

6. a) Find the Laplace Transform of

(i) $\frac{df}{dt}$

(ii) $\int f(t) dt$

5

- b) Find $i(t)$ by Laplace Transform if the Switch is closed at $t = 0$.

Assume that the capacitor is initially uncharged. 8

