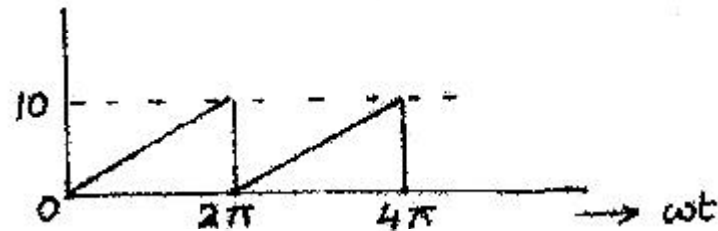


8. a) Find the fourier series for the waveform given below : 10



- b) Find out

10

$$\mathcal{L}^{-1} \left( \frac{s+5}{s^2+2s+5} \right)$$

## BACHELOR OF COMPUTER SC. ENGG. EXAMINATION, 2011

( 1st Year, 1st Semester, Old )


### CIRCUIT & NETWORK THEORY

Time : Three hours

Full Marks : 100

Answer *any five* questions

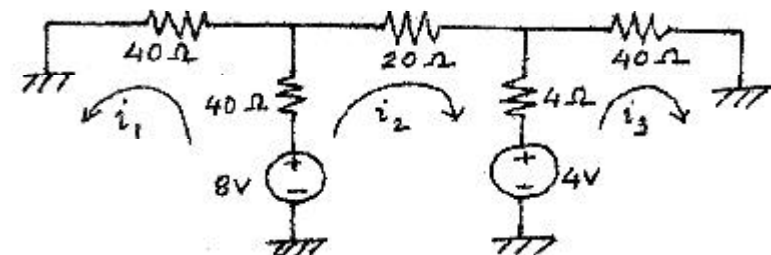1. a) A series RL circuit is connected to a battery of constant e.m.f. E. Derive the expression for current  $i$  in the circuit as a function of time. Also derive the expression for voltage across R and L. 10  
 b) A voltage  $v = 250 \cos(377t)$  is applied to a circuit of R and L in series.  $R = 7.00$  ohms and  $L = 63.7$  mH. Find V, Z, I and  $i$ . Derive the required Expressions. 10
2. a) State and prove the Maximum Power Transfer theorem for circuits with resistances and reactances. 10  
 b) Determine by delta-star conversion the total resistance of the following bridge circuit. 10
3. Given the following circuit.




[ Turn over

[ 2 ]

Calculate  $i_1$  and  $i_3$  by

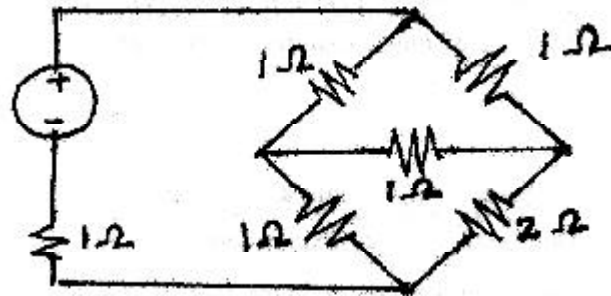- i) Mesh current method.
  - ii) Node voltage method.
4. a) Write the general equations for conversion from star to delta circuit and vice-versa. 10
- b) Given the following circuit.




If a battery of e.m.f.  $V$  is at A, what will be the current recorded by an ammeter at B ? What will happen if the position of the battery and the ammeter are interchanged ?

Hence state the Reciprocity theorem. 10


5. a) Draw the series RLC circuit and derive the expression for the following :
- i) Resonant frequency
  - ii) Bandwidth
  - iii) Values of impedance and reactance at resonance. 10

[ 3 ]

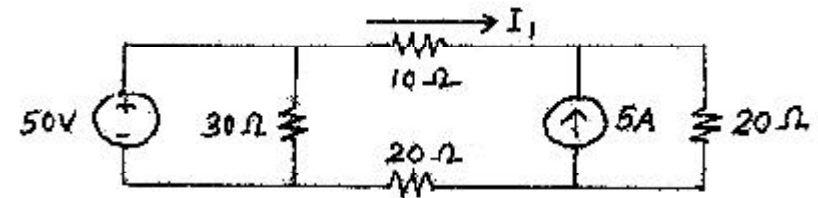- b) It is require that a series circuit of L, C, and R be resonant at 1 MHz. Its bandwidth is to be 5000 Hz. and impedance at resonance is to be 50 ohms. Find L, C, and R. 10
6. a) Obtain the current  $I_1$  in the 10 ohms resistor in the following circuit, using Superposition theorem. 10



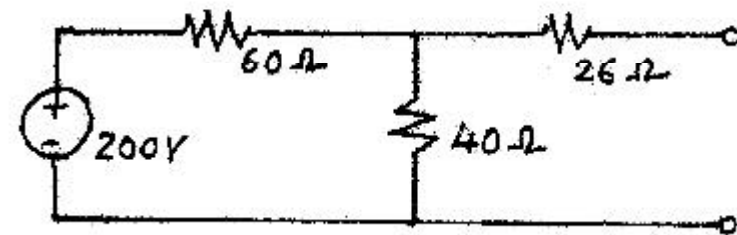- b) Replace the following circuit by its
- i) Thevenin's equivalent.
  - ii) Norton's equivalent. 10



7. a) Design one T-section low pass filter of constant - k type. Given that  $f_c = 2.5$  KHz and  $R_k = R = 10K$  ohms. 10
- b) Design one T-section high pass filter of constant - k type. Given that  $f_c = 2.5$  KHz and  $R_k = R = 10K$  ohms. 10

[ Turn over